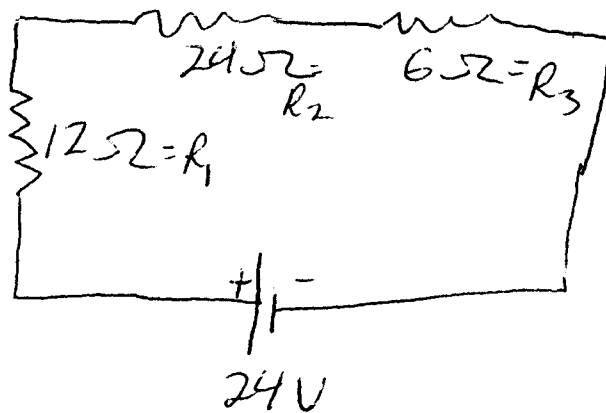


Electric Current + Circuits
Problems 38-42: Series Circuits

38



Current?

1st Find $R_{EQ} = R_1 + R_2 + R_3$

$$R_{EQ} = 12\Omega + 24\Omega + 6\Omega$$

$$R_{EQ} = 42\Omega$$

Use $V = IR$ to find I , $I = \frac{V}{R_{EQ}} = \frac{24V}{42\Omega}$

$I = 0.57A$
↑
for all resistors

Voltage Drops

$$V_1 = IR_1 = 0.57A \cdot 12\Omega = 6.84V \approx 6.9V$$

$$V_2 = IR_2 = 0.57A \cdot 24\Omega = 13.68V \approx 13.7V$$


$$V_3 = IR_3 = 0.57A \cdot 6\Omega = 3.42V \approx 3.4V$$

V_{total}

$$23.94V \approx 24V$$

①

39

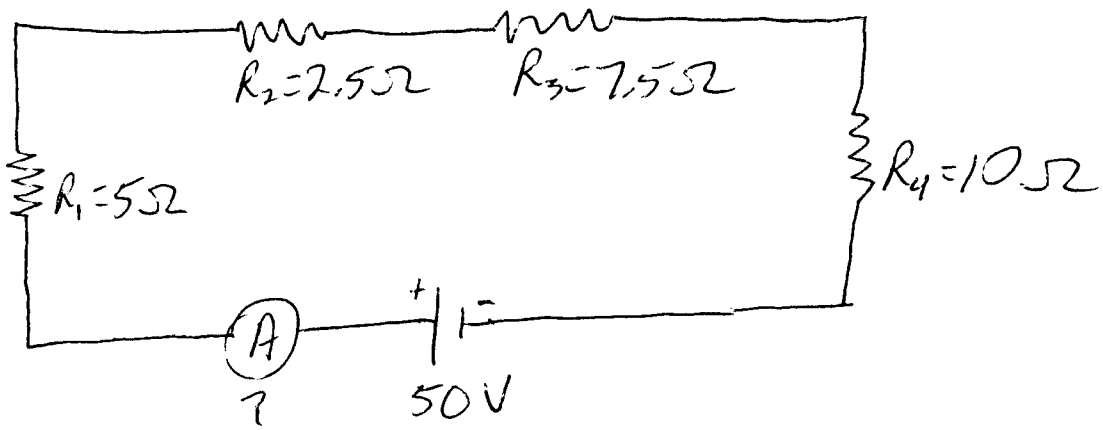

$$I = \frac{V}{R_{E2}} = \frac{50V}{(5\Omega + 2.5\Omega + 7.5\Omega + 10\Omega)} = \frac{50V}{25\Omega} = 2A$$

Current through each resistor

$$V_1 = IR_1 = 2A \cdot 5\Omega = 10V$$

$$V_2 = IR_2 = 2A \cdot 2.5\Omega = 5V$$


$$V_3 = IR_3 = 2A \cdot 7.5\Omega = 15V$$

$$V_4 = IR_4 = 2A \cdot 10\Omega = 20V$$

+
50V

2


~~39~~
40

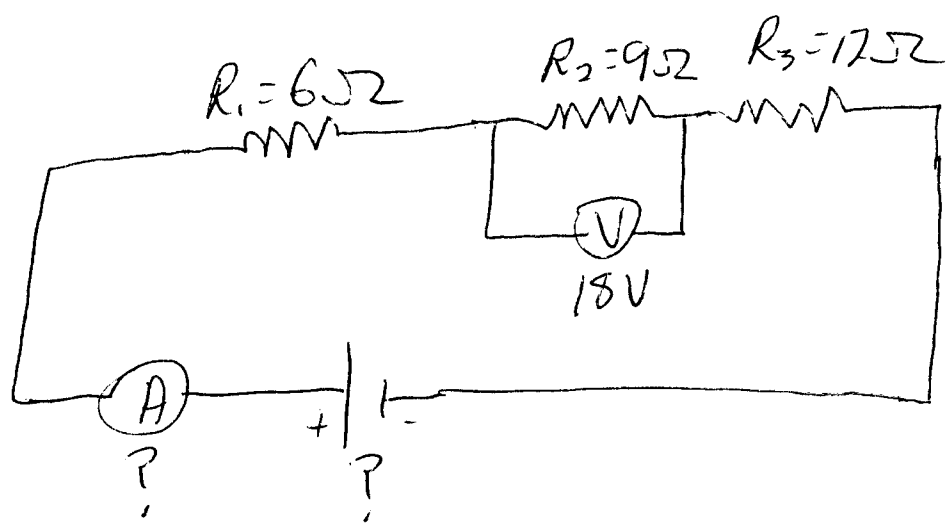

First find $I = \frac{V_2}{R_2} = \frac{18V}{9\Omega} = 2A$

$V_{\text{battery}} = IR_1 + IR_2 + IR_3$ or $I(R_1 + R_2 + R_3)$
 $2A(6\Omega + 9\Omega + 12\Omega) = 2A \cdot 27\Omega = 54V$


41

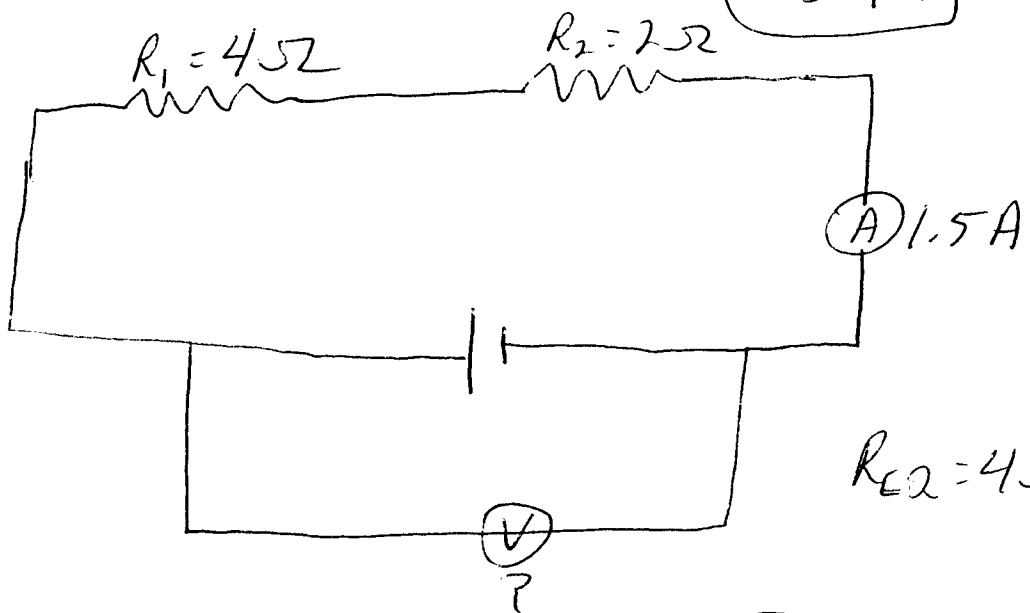

$R_{\text{eq}} = 4\Omega + 2\Omega = 6\Omega$

$V = IR_{\text{eq}} = 1.5A(6\Omega) = 9V$

(47)

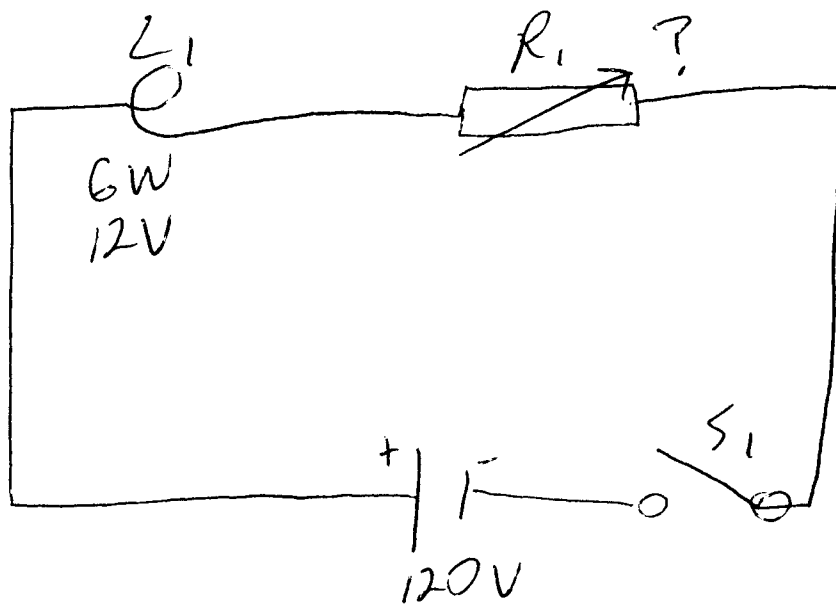

First, find current knowing that $P = 12V$.

$$\text{So } I = \frac{P}{V} = \frac{6 \frac{W}{V}}{12 \frac{V}{V}} = 0.5 \frac{W}{V} = \text{0.5A}$$

Voltage Drop across $R_1 = 120V - 12V = 108V$
 $R_{V_{total}} - V_{L1}$

$$R = \frac{V}{I} = \frac{108V}{0.5A} = 216\Omega$$

(4)